

25900783

Reg.No :

Name :

MAHATMA GANDHI UNIVERSITY, KOTTAYAM
MGU-BCA (HONOURS) REGULAR /IMPROVEMENT/ REAPPEARANCE
EXAMINATION NOVEMBER 2025

FIRST SEMESTER

Core Course (CC) - MG1CCRBCA100 - DIGITAL FUNDAMENTALS
(2024 ADMISSION ONWARDS)

Duration: 2 Hours

Maximum Marks: 70

Remember(K), Understand(U), Apply(A), Analyse(An), Evaluate(E), Create(C), Skill(S), Interest(I) and Appreciation(Ap)

Students should attempt at least one question from each course outcome to enhance their overall outcome attainability.

Part A

Very Short Answer Questions

Answer **All** Questions

Each Question carries **2** marks

1. Explain the process of converting a decimal number to binary. [U] / [CO1]
2. Explain the concept of overflow in binary addition. [U] / [CO1]
3. Convert the expression into sum-of-product (SOP) form- $(A+B)(A+B+C)$. [A] / [CO2]
4. Simplify the expression $f = A + B[AC + (B + C') D]$ using basic laws of Boolean algebra. [A] / [CO2]
5. What is the use of a de-multiplexer? [K] / [CO3]
6. Draw the block diagram of a combinational logic circuit. [U] / [CO3]
7. Define sequential circuits and explain their significance. [U] / [CO4]
8. Explain the concept of toggling in a JK flip-flop. [U] / [CO4]
9. Convert the binary number 101011 to octal. [A] / [CO1]

10. What is the primary difference between a half adder and a full adder? [U] / [CO3]

[10x2 = 20]

Part B

Short Answer Questions

Answer any **5** out of **7** Questions

Each Question carries **6** marks

11. Convert the decimal number 357 to its BCD representation using the 8421 code. Show each step of the conversion process. [A] / [CO1]

12. Simplify the expression $F(x,y,z)=\Sigma(0,6)$ and implement with NOR gate. [A] / [CO2]

13. Explain how a decoder is used for memory address selection in computer systems. [U] / [CO3]

14. Discuss the characteristics and use of a D flip-flop. [U] / [CO4]

15. Compare and contrast the binary, octal, and hexadecimal number systems. Discuss the benefits of each in computing. [U] / [CO1]

16. Apply De Morgan's theorems to each of the following expressions (i) $[(A + B + C) D]'$ (ii) $(ABC + DEF)'$ (iii) $(AB' + C'D + EF)'$. [A] / [CO2]

17. Compare the behaviour of positive-edge-triggered and negative-edge-triggered flip-flops based on a timing diagram. [An] / [CO4]

[5x6 = 30]

Part C

Essay Questions

Answer any **2** out of **3** Questions

Each Question carries **10** marks

18. Simplify the Boolean function using K-Map:
 $F(w,x,y,z)=\Sigma(1,3,4,5,6,9,12,13)$. [A] / [CO2]

19. Design an 8×1 multiplexer using 4×1 and 2×1 multiplexer. [A] / [CO3]

20. Describe the operation of a 4-bit serial-in parallel-out (SIPO) shift register. Include a timing diagram to show how data is shifted in and read out. [U] / [CO4]

[2x10 = 20]